



INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY

H Y D E R A B A D

INTERNATIONAL INSTITUTE OF INFORMATION TECHNOLOGY
HYDERABAD

VLSI Design Project

Course Code: M25EC2

November - 25

Ravi Kumar Sahu

Student ID: 2024102024

Contents

I	Introduction	i
II	Concepts CLA	i
III	Logic Gate Requirements	ii
IV	Topology and Sizing	iii
IV.i	Logic Gate Sizing	iii
IV.ii	Flip-Flop Topology	iii
V	Timing Analysis Theory	iii
VI	PreLayout Analysis	iv
VI.i	Inverter	iv
VI.i.1	Delay Analysis	iv
VI.ii	DFF	v
VI.ii.1	Dealy Analysis	v
VI.iii	Propagator and Generator	vi
VI.iv	CLA Block	ix
VI.v	Final Adder	xi
VI.vi	Summary PreLayout	xvii
VII	Post Layout Work	xvii
VII.i	Magic Layout	xvii
VII.ii	Magic Layout	xviii
VII.ii	Post Layout Simulation	xxv
VII.iii.1	Critical Path Delay A=11111 , B=00001	xxxvii
VII.iv	Delay analysis	xl
VIII	Verilog	xlii
IX	RTL Simulation	xliii

Abstract

The Carry Look-Ahead (CLA) Adder is designed and implemented using 180nm CMOS technology, reducing propagation delay through hierarchical blocks. Validated using NGSPICE simulations and MAGIC layouts, the design is verified post-layout. A Verilog-based structural description enables FPGA implementation for hardware validation. Key performance metrics, including delay, maximum frequency, and power efficiency, demonstrate the CLA adder's high-speed and reliable operation. **Keywords**—CLA, NGSPICE, MAGIC, Delay, Verilog, FPGA

I Introduction

The Carry Look-Ahead Adder (CLA) is an improved version of the Ripple Carry Adder (RPA). The primary disadvantage of the RPA is the carry propagation delay, where the most significant bit must wait for the carry signal to ripple through all previous stages. In this 5-bit design, the input bits are defined as A_i and B_i (where $i = 0$ to 4) along with an initial carry C_0 . The CLA solves the delay problem by pre-computing carries in parallel rather than waiting for the sequential ripple effect.

Sequential dependency is effectively removed by computing the Propagate (P_i) and Generate (G_i) signals for each bit independently. The fundamental logic for these signals is defined as:

$$P_i = A_i \oplus B_i \tag{1}$$

$$G_i = A_i \cdot B_i \tag{2}$$

The sum bits (S_i) are subsequently calculated as:

$$S_i = P_i \oplus C_i \tag{3}$$

Positive edge-triggered flip-flops are used to provide stable inputs and capture the outputs. If input bits are available before the rising edge of the clock, the output is computed and latched at the next rising edge.

II Concepts CLA

The carry for any stage $i + 1$ is derived from the generate and propagate terms of the previous stage according to the equation $C_{i+1} = G_i + (P_i \cdot C_i)$.

For the implemented 5-Bit CLA, the carry equations are expanded to compute C_1 through C_5 in parallel. This architecture removes the wait time associated with ripple adders. The expanded boolean equations are:

$$\begin{aligned}
C_1 &= G_0 + P_0 \cdot C_0 \\
C_2 &= G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_0 \\
C_3 &= G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_0 \\
C_4 &= G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0 \\
&\quad + P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0 \\
C_5 &= G_4 + P_4 \cdot G_3 + P_4 \cdot P_3 \cdot G_2 + P_4 \cdot P_3 \cdot P_2 \cdot G_1 \\
&\quad + P_4 \cdot P_3 \cdot P_2 \cdot P_1 \cdot G_0 + P_4 \cdot P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_0
\end{aligned}$$

As demonstrated by the equation for C_5 , the hardware complexity and fan-in requirements increase with the bit-width. The final term requires a 6-input AND gate and the summation requires a 6-input OR gate.

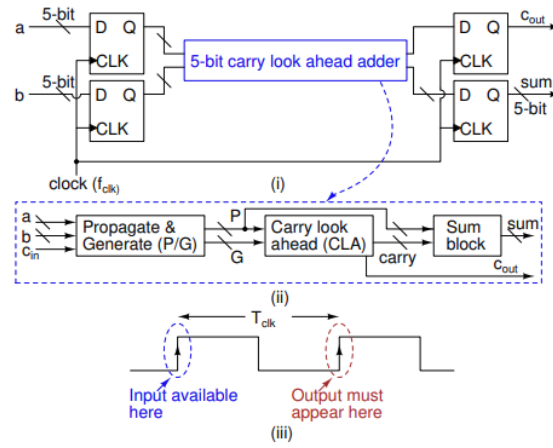


Figure 1

Figure 1: figure-noName

III Logic Gate Requirements

To implement the 5-Bit CLA logic based on the derived equations, the following specific logic gates are required:

- **NOT Gate**
- **XOR Gate:** 2-input (for Sum generation).
- **AND Gates:** 2, 3, 4, 5, and 6-input configurations.
- **OR Gates:** 2, 3, 4, 5, and 6-input configurations.

The inclusion of 6-input AND and OR gates is a specific requirement for the 5-bit design to handle the C_5 carry generation term, which involves propagating the carry logic through the five preceding stages (0 to 4).

All logic gates have been designed using the Complementary CMOS logic style. The input and output D flip-flops are designed using True-Single-Phase-Clock (TSPC) topology. The overall design utilizes a 3-stage structure where the 1st and 3rd stages are flip-flops for signal stability, and the 2nd stage is the combinational CLA block.

IV Topology and Sizing

The circuit is implemented using 180nm technology with a minimum feature size (λ) of $0.09\mu m$. The sizing strategy aims to balance rise and fall times by compensating for the lower mobility of PMOS carriers compared to NMOS carriers.

IV.i Logic Gate Sizing

- **NOT Gate:** Standard sizing is used with $W_N = 10\lambda$ and $W_P = 20\lambda$.
- **AND Gates:** Implemented by cascading a NAND gate with an inverter. The NMOS widths in the NAND stack are multiplied by the number of inputs (N) to maintain equivalent pull-down strength. For the 5-bit design, this extends up to a 6-input NAND where $W_N = 6 \times W_{ref}$.
- **OR Gates:** Implemented by cascading a NOR gate with an inverter. The PMOS widths in the NOR stack are multiplied by the number of inputs (N) to maintain equivalent pull-up strength. For the 6-input case, $W_P = 6 \times W_{ref}$.

IV.ii Flip-Flop Topology

The D flip-flops utilize the TSPC (True-Single-Phase-Clock) topology. This dynamic logic style is chosen to reduce the transistor count and clock load compared to static CMOS flip-flops.

V Timing Analysis Theory

The performance of the 5-bit CLA is evaluated based on the following timing parameters:

- **Setup Time (T_{setup}):** The minimum time interval before the clock's active edge during which the data input must remain stable. This is determined by changing the D input just before the rising edge of the clock.
- **Hold Time (T_{hold}):** The minimum time interval after the clock's active edge during which the data input must remain stable. For the TSPC flip-flop topology used, the theoretical hold time is approximately 0 ps.
- **Clock-to-Q Delay (T_{cq}):** The time delay between the active edge of the clock and the valid output appearing at Q.
- **Propagation Delay (T_{pd}):** The time required for the combinational logic (CLA block) to produce a valid sum and carry output after the inputs change. This is measured by identifying the maximum rise and fall delays for the worst-case input transitions (e.g., propagating a carry from bit 0 to bit 5).

VI PreLayout Analysis

VI.i Inverter

```
Measurements for Transient Analysis
tpcq_inv      = 1.765958e-11 targ= 5.032660e-09 trlg= 5.015000e-09
```

Figure 2: Propagation delay analysis for the CMOS inverter.

 


Figure 3: Voltage transfer characteristics (VTC) and transient plot of the inverter.

VI.i.1 Delay Analysis

The Delay of this Inverter is **17.66ps**

VI.ii DFF

 


Figure 4: Transient response plot of the D-Flip Flop.

 


Figure 5: Analysis of the propagation delay for the D-Flip Flop.

VI.ii.1 Dealy Analysis

Measurement	Value (ps)
tpcq_lh (LH)	2495.99ps
tpcq_hl (HL)	144.70ps
avg_tpcq (average)	1320ps

VI.iii Propagator and Generator

 


Figure 6: reference diagram

 


Figure 7: Propagate and Generate signal outputs for Bit 1.

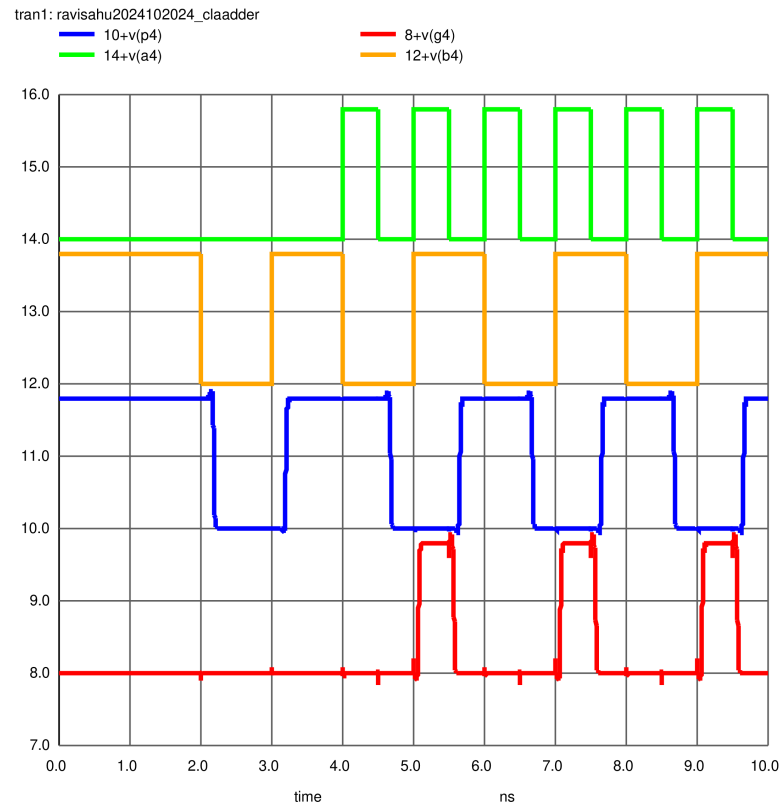


Figure 8: Propagate and Generate signal outputs for Bit 4.

Measurement	Value (ps)
prop_delay	154.03ps
gen_delay	65.13ps

VI.iv CLA Block

 


Figure 9: Input signals entering the Carry Look-Ahead (CLA) block.

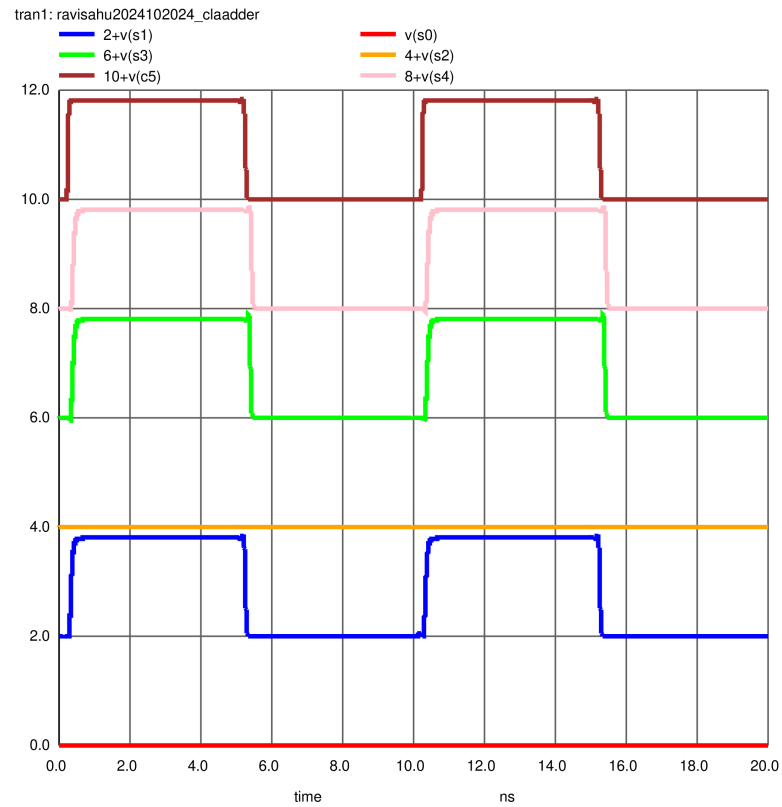


Figure 10: Output signals generated by the Carry Look-Ahead (CLA) block.

Measurement	Value (ps)
tpcq_cla	401.32ps

VI.v Final Adder

 


Figure 11: Waveform of the final generate signals for the adder circuit.

 


Figure 12: Outputs of the input D-Flip Flops feeding into the adder logic.

 


Figure 13: Initial input signals applied to the adder testbench.

 


Figure 14: Captured output signals from the final D-Flip Flops.

 


Figure 15: Waveform of the propagate signals within the adder logic.

 


Figure 16: Final Sum and Carry outputs of the adder.

Measurement	Value (ps)
delay_dff_in	96.30ps
delay_cla	432.99ps
delay_dff_out	47.46ps
total_delay	576.75ps

Stage	Delay (ps)	Percentage of Total
Stage 1 - Input DFF	96.30ps	16.7%
Stage 2 - CLA Core	432.99ps	75.1%
Stage 3 - Output DFF	47.46ps	8.2%
Total Path Delay	576.75ps	100%

VI.vi Summary PreLayout

Circuit	Key Delay	Value (ps)	Value (ns)
Inverter	tpcq_inv	17.66	0.01766
D Flip-Flop	tpcq_lh (rise)	2495.99	2.496
D Flip-Flop	tpcq_hl (fall)	144.70	0.1447
D Flip-Flop	avg_tpcq	1320.00	1.320
CLA Block	tpcq_cla	401.32	0.40132
Full Adder (Input)	delay_dff_in	96.30	0.0963
Full Adder (Core)	delay_cla	432.99	0.4330
Full Adder (Output)	delay_dff_out	47.46	0.0475
Full Adder (Total)	total_delay	576.75	0.5768
Prop/Gen (Prop)	prop_delay	154.03	0.15403
Prop/Gen (Gen)	gen_delay	65.13	0.06513

VII Post Layout Work

VII.i Magic Layout

In the design of a 5-bit Carry Lookahead Adder (CLA) using the magic layout methodology, the approach builds upon modular propagate and generate cells that are consistently reused across different bit-widths (2-, 3-, 4-, 5-, and 6-bit). Each bit cell computes the propagate ($P_i = A_i \oplus B_i$) and generate ($G_i = A_i \cdot B_i$) signals, which are then combined to form the carry equations. The carry logic follows the standard lookahead formulation:

$$C_{i+1} = G_i + P_i \cdot C_i,$$

with higher-order carries expanded hierarchically, e.g.,

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0.$$

By verifying the base propagate/generate unit once, the same layout can be replicated and tiled to construct larger CLAs without redesigning the logic. For the 5-bit case, five identical propagate/generate cells are placed in sequence, with careful alignment of diffusion regions and metal layers to minimize parasitic capacitances and interconnect delay. This modularity ensures reproducibility and scalability: the same generator and propagator templates are reused across different bit-width designs, yielding a consistent and optimized carry path suitable for implementation.

VI. STICK DIAGRAMS

 


Fig. 21. D Flip-Flop

 


Fig. 24. Inverter

 


Fig. 22. AND Gate (Generate)

 


Fig. 25. CARRY 2

 


Fig. 23. XOR Gate (Propagate)

 


Fig. 26. CARRY 3

 


Fig. 27. CARRY 4

VII.ii Magic Layout

 


Figure 17: Magic layout for and2

 


Figure 18: Magic layout for and3

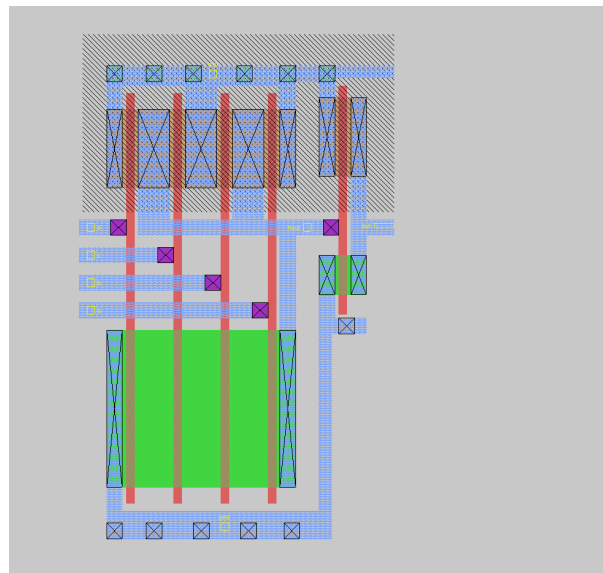


Figure 19: Magic layout for and4

 


Figure 20: Magic layout for and5

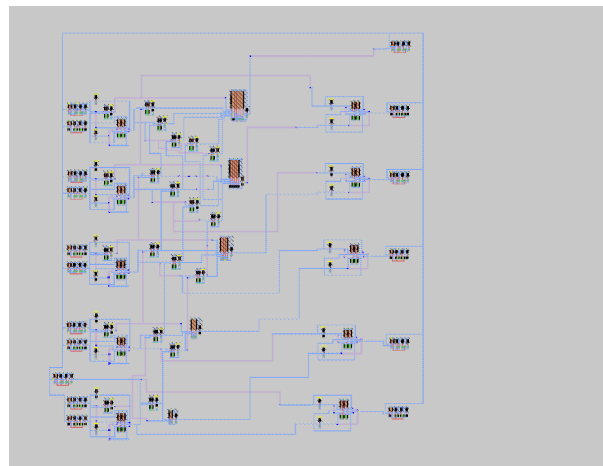


Figure 21: Magic layout for claFinal

 


Figure 22: Magic layout for dff.png

 


Figure 23: Magic layout for inv

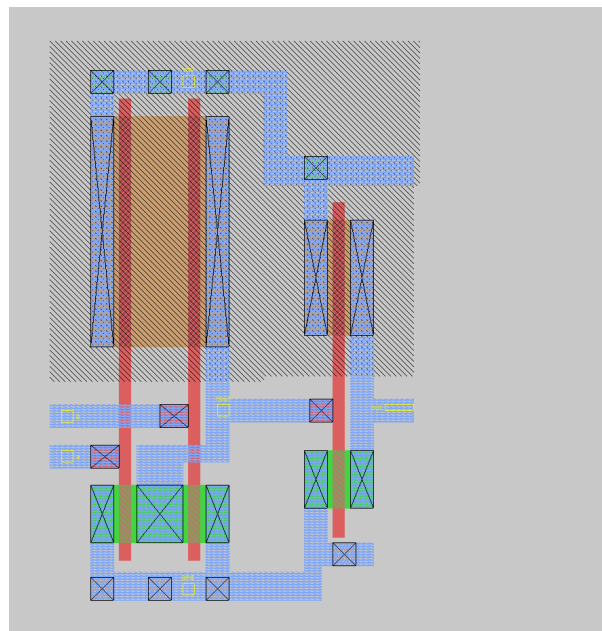


Figure 24: Magic layout for or2

 


Figure 25: Magic layout for or3

 


Figure 26: Magic layout for or4

 


Figure 27: Magic layout for or5

 


Figure 28: Magic layout for or6

 


Figure 29: Magic layout for XorPost

VII.iii Post Layout Simulation

 


Figure 30: Post-layout simulation waveform for the 2-input AND gate.

 


Figure 31: Post-layout simulation waveform for the 3-input AND gate.

 


Figure 32: Post-layout simulation waveform for the Inverter (INV).

 


Figure 33: Post-layout simulation waveform for the 4-input OR gate.

 


Figure 34: Post-layout simulation waveform for the 6-input OR gate.

 


Figure 35: Post-layout simulation waveform for the XOR gate.

 


Figure 36: Post-layout simulation waveform for the D Flip-Flop (DFF).

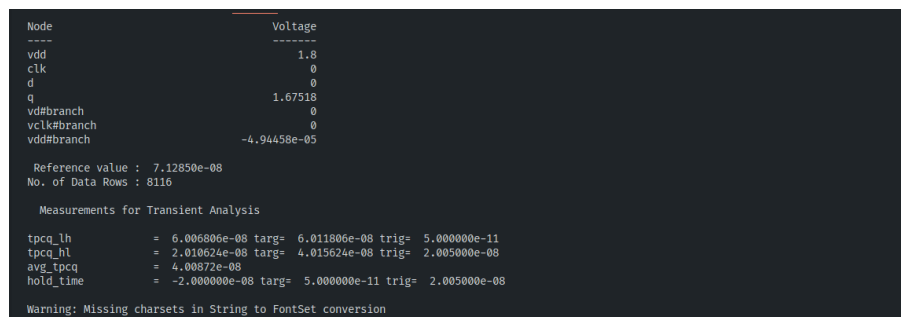


Figure 37: Hold Time

 


Figure 38: Final output waveform for the 0th bit of the Carry Look-Ahead (CLA) adder.

 


Figure 39: Final output waveform for the 1st bit of the Carry Look-Ahead (CLA) adder.

 


Figure 40: Final output waveform for the 2nd bit of the Carry Look-Ahead (CLA) adder.

 


Figure 41: Final output waveform for the 3rd bit of the Carry Look-Ahead (CLA) adder.

 


Figure 42: Final output waveform for the 4th bit of the Carry Look-Ahead (CLA) adder.

VII.iii.1 Critical Path Delay A=11111 , B=00001

 


Figure 43: input A

 


Figure 44: input B

 


Figure 45: Carry Out (C)

 


Figure 46: Sum Out (S)

VII.iv Delay analysis

XOR GATE				
Input	Pin	Rise	Fall	Average
Input A	a	10159.43 ns	0.0452 ps	5102.33 ns
Input B	b	10159.43 ns	-19954.78 ps	-4897.67 ns

D FLIP-FLOP				
[Clock-to-Q measurements]				
Signal	Pin	Rise (ps)	Fall (ps)	Average (ps)
Clock	clk	60067.06	20106.24	40087.15
SetupTime	t_{setup}	2 ns		

CLA [Sum outputs S0-S3, Carry output C5]				
Output	Pin	Rise (ps)	Fall (ps)	Average (ps)
Sum Bit 0 (S0)	s0	60456.31	-19700.34	20377.98
Sum Bit 1 (S1)	s1	60516.97	-19490.64	20513.16
Sum Bit 2 (S2)	s2	20797.46	-19453.23	672.11
Sum Bit 3 (S3)	s3	60474.01	-19464.47	20504.76
Sum Bit 4 (S4)	s4	60500.00	-19531.97	20484.02
Carry Out (C5)	c5	60500.00	-19500.00	20500.00

VIII Verilog

```
iverilog -o cla_sim cla.v cla_tb.v 86 vvp cla_sim
VCD info: dumpfile dump_cla_adder.vcd opened for output.
Time=0 a_in=00000 b_in=00000 cin=0 sum=xxxxx cout=x
Time=7 a_in=00000 b_in=00000 cin=0 sum=xxxxx cout=0
Time=21 a_in=00000 b_in=00000 cin=0 sum=00000 cout=0
Time=105 a_in=00001 b_in=00001 cin=0 sum=00000 cout=0
Time=119 a_in=00001 b_in=00001 cin=0 sum=00010 cout=0
Time=217 a_in=01111 b_in=00001 cin=0 sum=00010 cout=0
Time=231 a_in=01111 b_in=00001 cin=0 sum=10000 cout=0
Time=329 a_in=10101 b_in=01010 cin=0 sum=10000 cout=0
Time=343 a_in=10101 b_in=01010 cin=0 sum=11111 cout=0
Time=441 a_in=10000 b_in=01111 cin=0 sum=11111 cout=0
Time=553 a_in=11111 b_in=11111 cin=0 sum=11111 cout=1
Time=567 a_in=11111 b_in=11111 cin=0 sum=11110 cout=1
cla_tb.v:58: $finish called at 753 (1s)
```

Figure 47: Verilog Output

 


Figure 48: WaveForm

IX RTL Simulation



Figure 49: Add 11111+11111

 


Figure 50: Add $10101+01010$



Figure 51: Add $11000+11100$